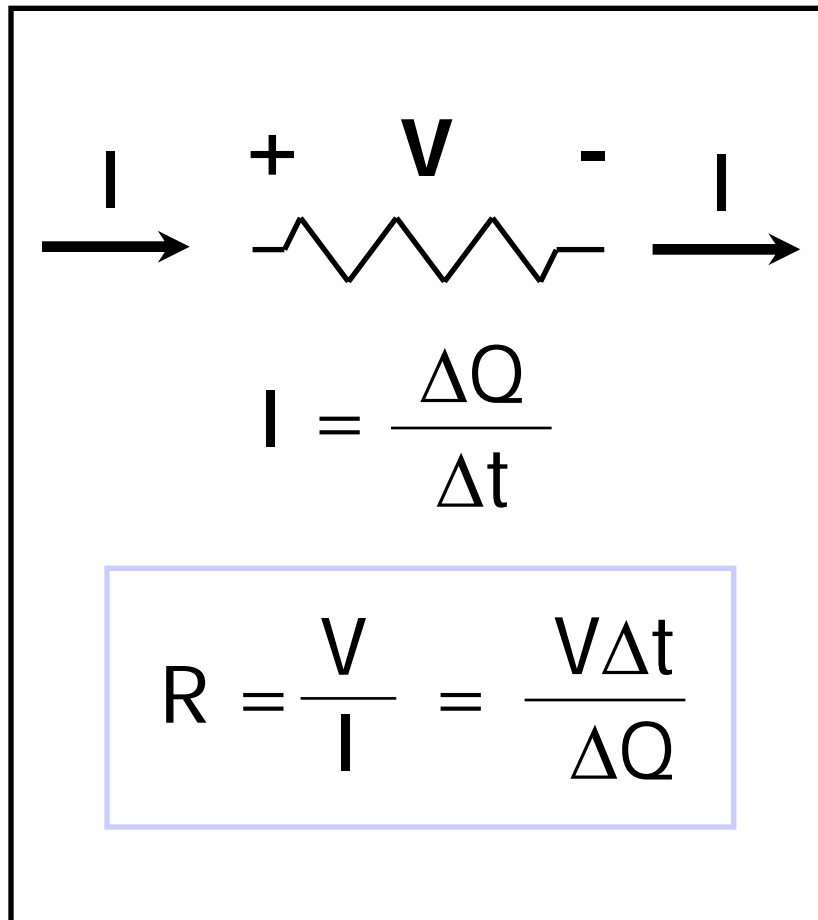


# Switched Capacitor: Sampled Data Systems


- **Basic switched capacitor theory**
- **How has Anadigm utilised this.**

# Resistor & Charge Relationship



- Resistance is defined in terms of current (I) and voltage (V).
- Current is the rate of change of charge.
- $R = V/I$

# Switching Charge to a Capacitor

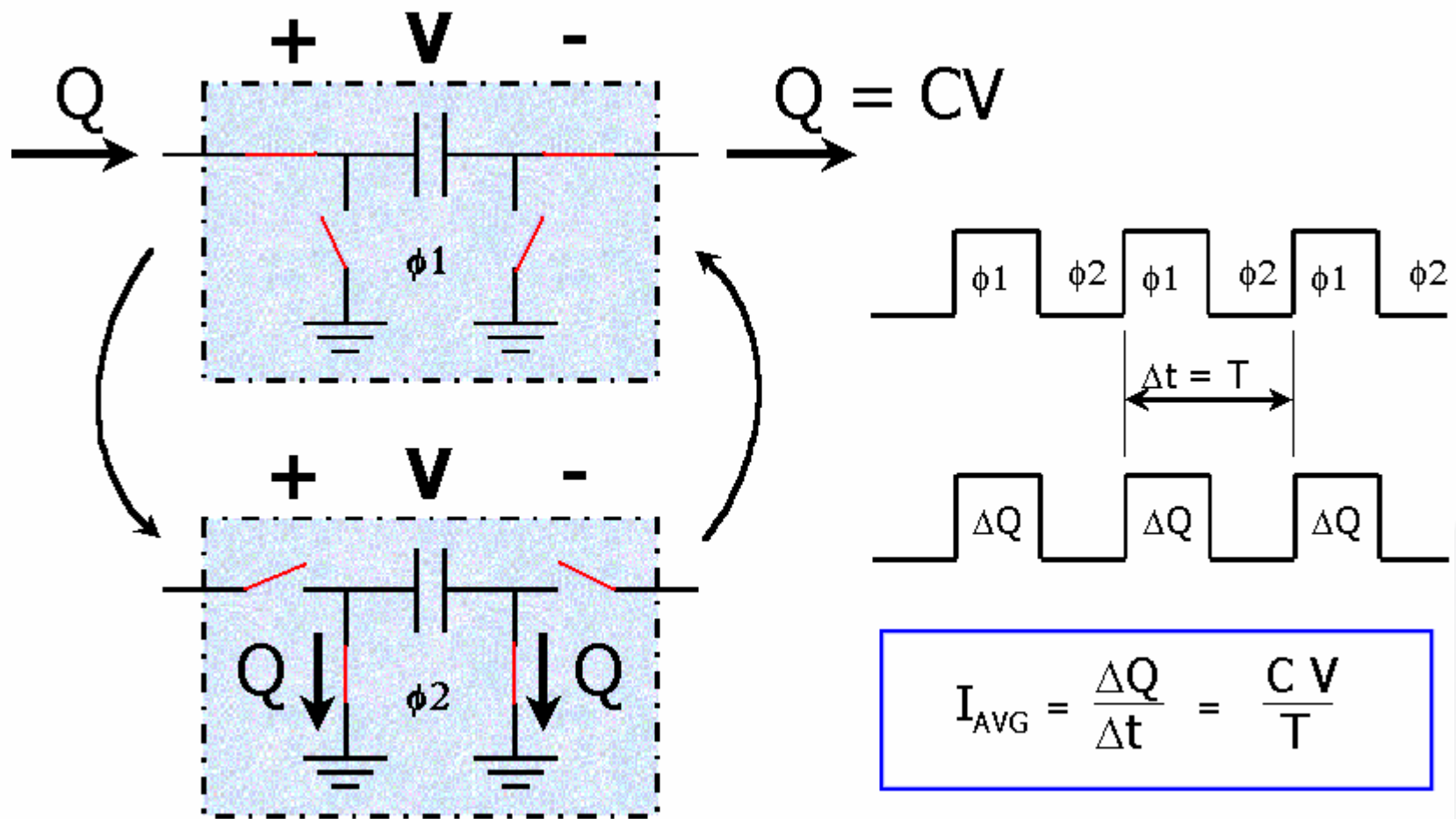

# Switched Capacitor as a Resistor

$$R = \frac{V}{I} = \frac{\cancel{V} T}{C \cancel{V}}$$

$$R = \frac{T}{C} = \frac{1}{fC}$$



$$\frac{R_1}{R_2} = \frac{\cancel{C_2} T}{\cancel{T} C_1} = \frac{C_2}{C_1}$$

- **Equivalent resistance**
  - Contains no “R”
  - Goes UP↑ as C goes down↓
  - Function only of “C” and clock period (T)
- **Ratios**
  - Independent of clocks
  - Depends on capacitor matching

# Why Switched Capacitor?

- **RC constants with only C's**
- **Area savings - much smaller for large "R"**
- **Better "resistor" values**
  - Better tolerance; typically  $\pm 1.0\%$
  - Better matching - typically  $\pm 0.1\%$
  - Better Linearity
  - Wider range
- **The "extras"**
  - Phase swapping
  - Frequency dependent *RC*'s


# Phase Swapping

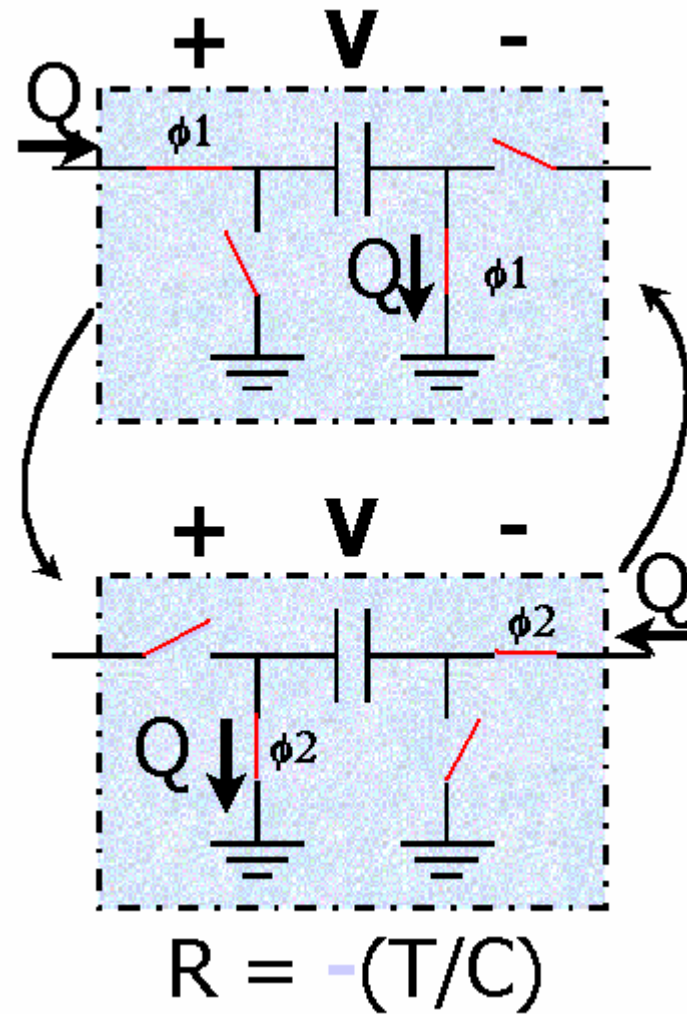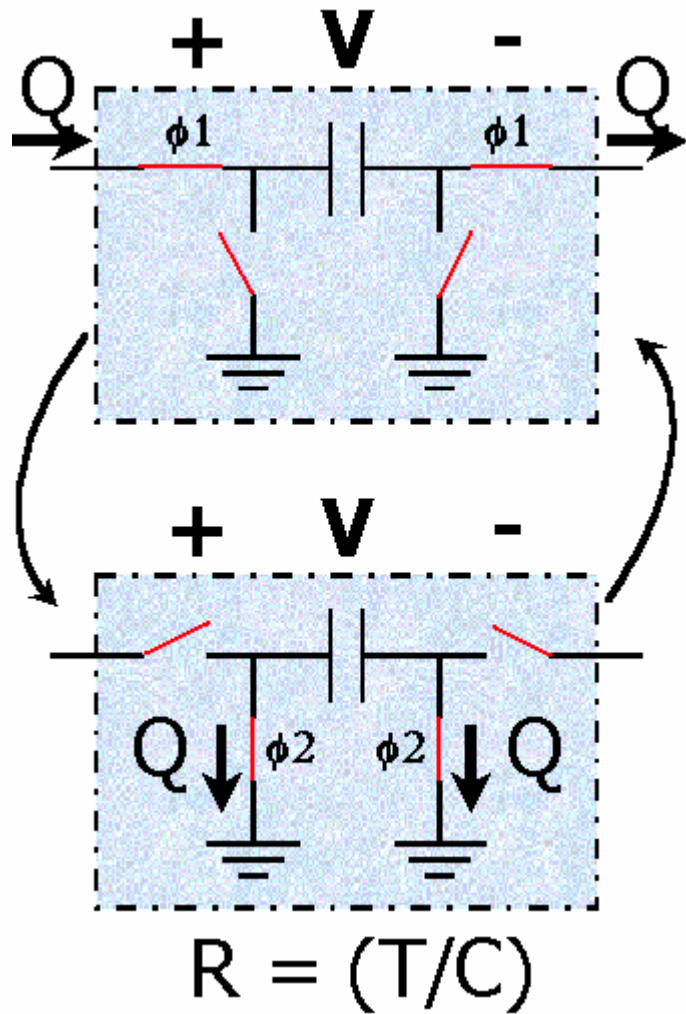

# The Clock as a System Reference




$$f_0 = 1/(RC)$$

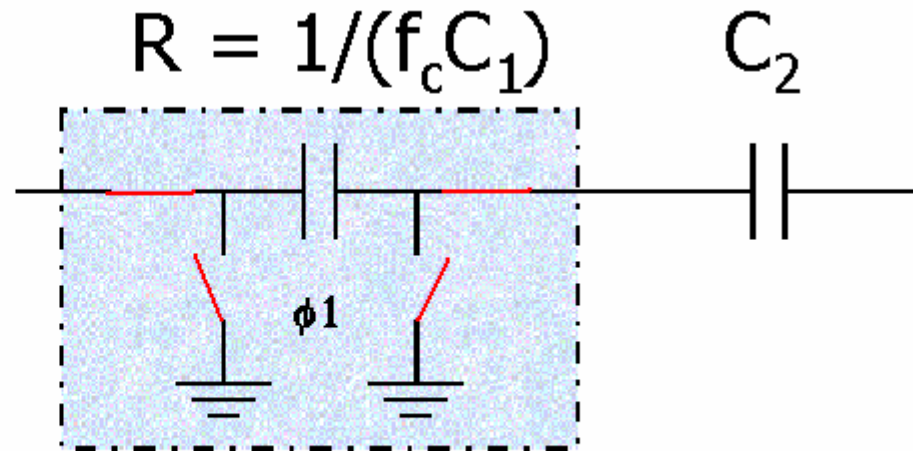


$$f_0 = 1/(RC_2) = f_c(C_1/C_2)$$

- **Corner frequency can be changed by changing the clock frequency**
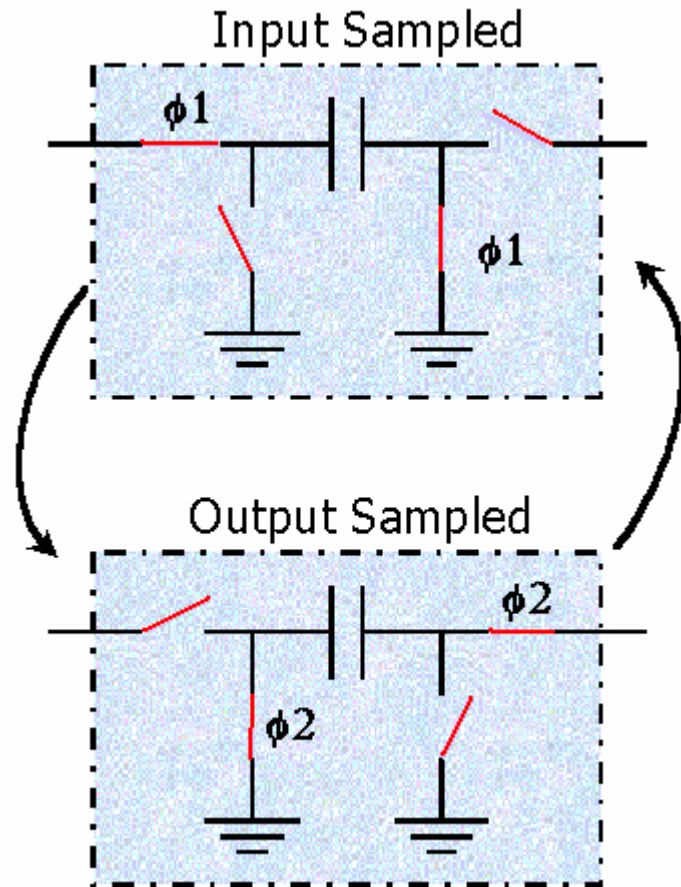
# Switched Capacitor Circuits are Sampled Data Systems





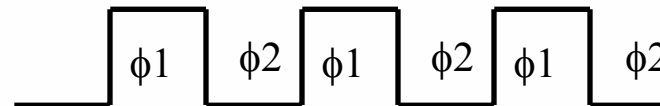- **Inputs and outputs may be valid only on certain phases**
- **Subject to sampled data system constraints**






# Expression of Sampled Data Function

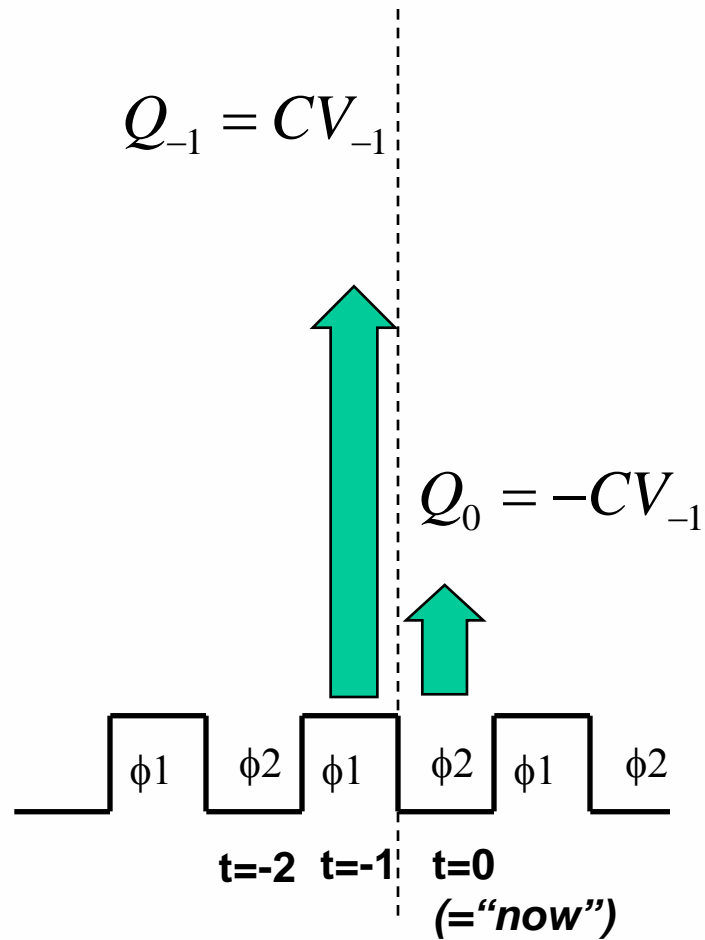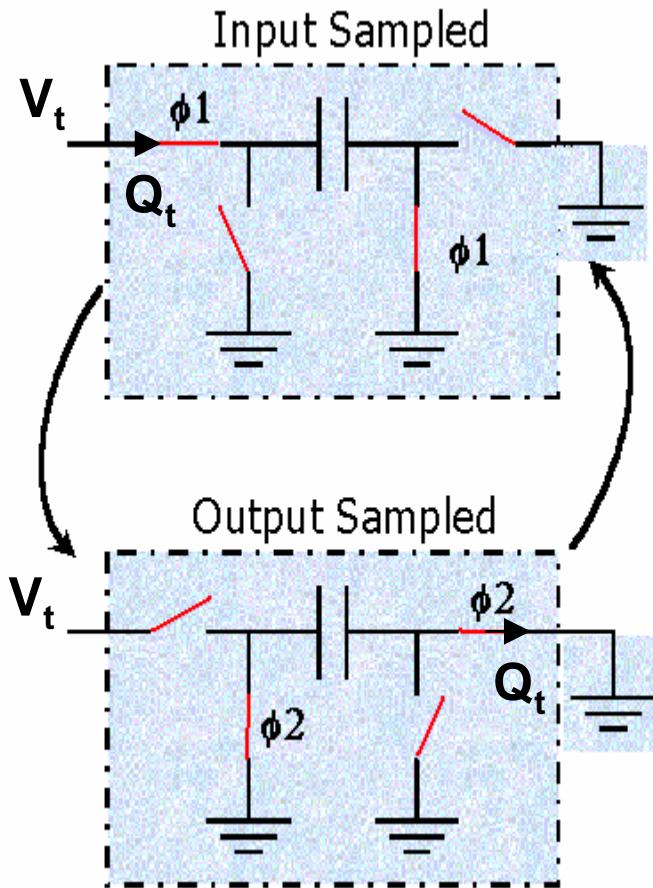

# Sampled Data Example...

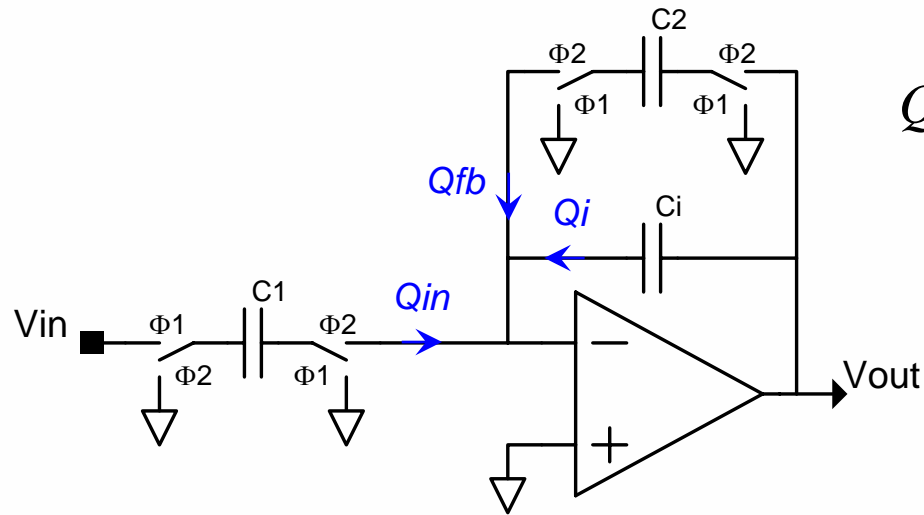


$$Qfb_0 = C2 \cdot Vout_0$$

$$Qi_0 = Ci \cdot (Vout_0 - Vout_{-1})$$

$$Qin_0 = -C1 \cdot Vin_{-1}$$

$$-C1 \cdot Vin_{-1} + C2 \cdot Vout_0 + Ci \cdot (Vout_0 - Vout_{-1}) = 0$$
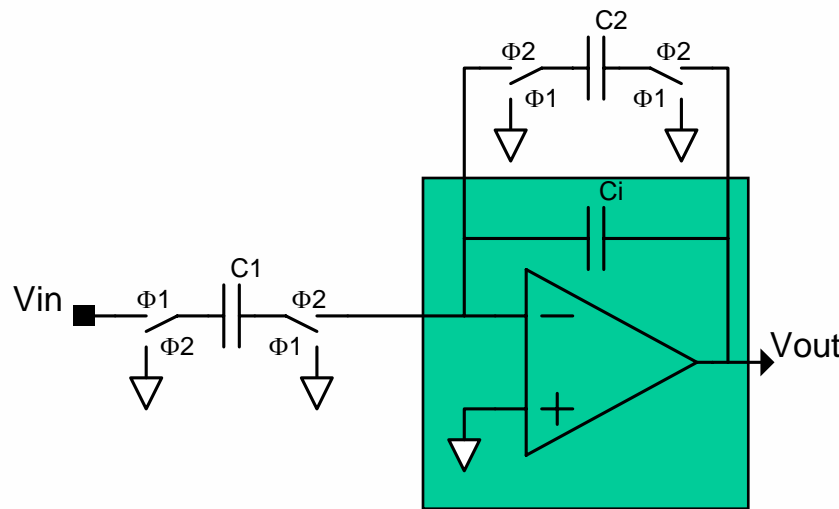
# ...And we get : AnadigmDesigner Simulator Equation!



All SC functions are about **ratios** of capacitors. Normalise all caps connected to an integrator stage to the integrator cap ( $=C_2$  here). So:

$$nC_i = 1 \quad nC_1 = \frac{C_1}{C_i} \quad nC_2 = \frac{C_2}{C_i}$$

On  $\phi_2$  :

$$Vout_0 = \frac{1}{(1 + nC_2)} \cdot (Vout_{-1} + nC_1 Vin_{-1})$$


On  $\phi_1$  :

$$Vout_0 = Vout_{-1}$$

# Performance: Programming Boundaries

- **Op-amp dynamics**
  - Gain-bandwidth product
  - Op-amp slew rate
  - Loading limits
- **Input offset**
- **Limit on filter order**
- **Capacitance spread**

# Opamp Gain Bandwidth Product

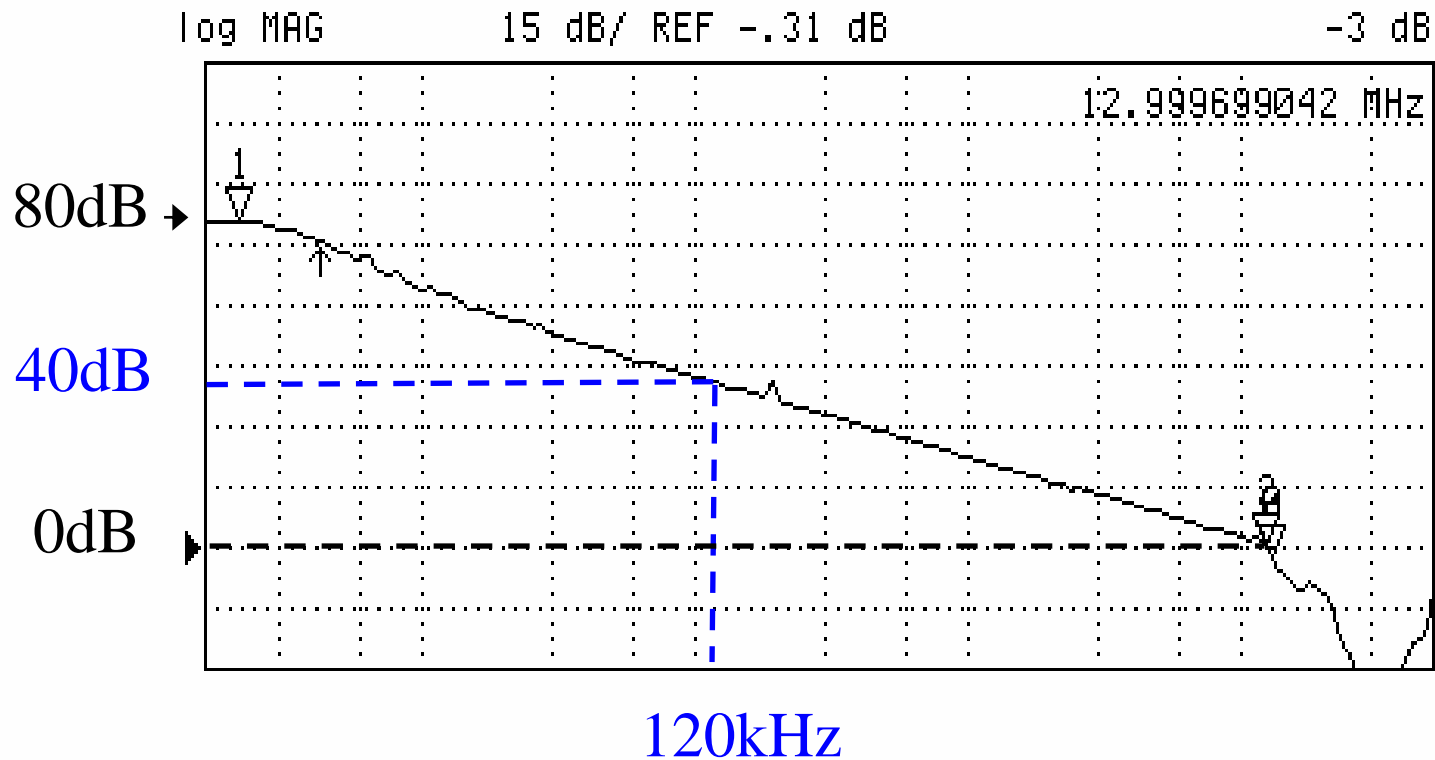


- There is a natural trade-off between bandwidth and gain
- This knowledge is built into the IPmodules

# Op-amp Slew Rate

- **Defines speed at which large transitions in output voltage are made.**
- **The op-amp is no longer operating in small-signal mode (the 'virtual ground' is destroyed temporarily)**
- **This is *separate to* GB product**
- **It arises from internal features of the op-amp, and is not a feature of capacitive loading**
  - Note: excess capacitive load causes op-amp instability (ringing)
  - Anadigm op-amp's are designed to drive 100pF load at unity gain
    - About 6 or 7 full-size input caps

# Input Offset

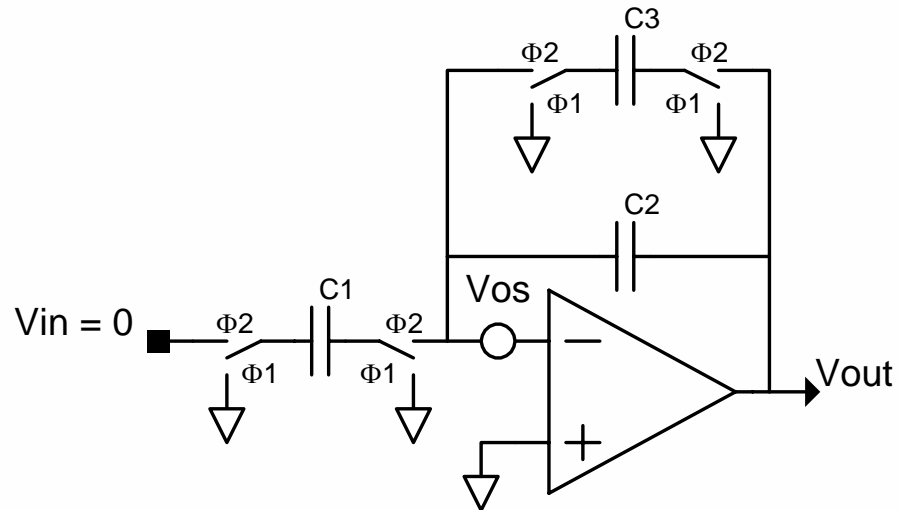

$$V_{out} = V_{os} \cdot \frac{(C_1 + C_3)}{C_3}$$

- Anadigm 3.3volt products have an internal offset “nulling” circuit this reduces the effective offset from a few mil-volts to less than 250 microvolts.
- 5 volt products do not have this feature

# Filter Order


- In theory, very large filters can be constructed with Anadigm's dpASP and FPAA products, 8 poles with each device and multiple devices can be used.
- All the previous effects are *cumulative* and will put a practical limit on filters that can be built.
- A rule of thumb, a maximum order of about 10-12 can be realised without special consideration of the second order effects mentioned previously (e.g. C-message telecoms filter)
  - Higher order filters with poles in their transfer function (IIR filters) are not often called for anyway.



# Capacitance Spread

- **The ratio of  $C_{\max}$  to  $C_{\min}$  in a given Switched Capacitor stage**
- **Limits CAM parameter ranges**
  - Lowest filter cut-off frequency
  - Minimum and maximum gain settings
  - Maximum length of integrator time-constant

# Extending Capacitance Spread

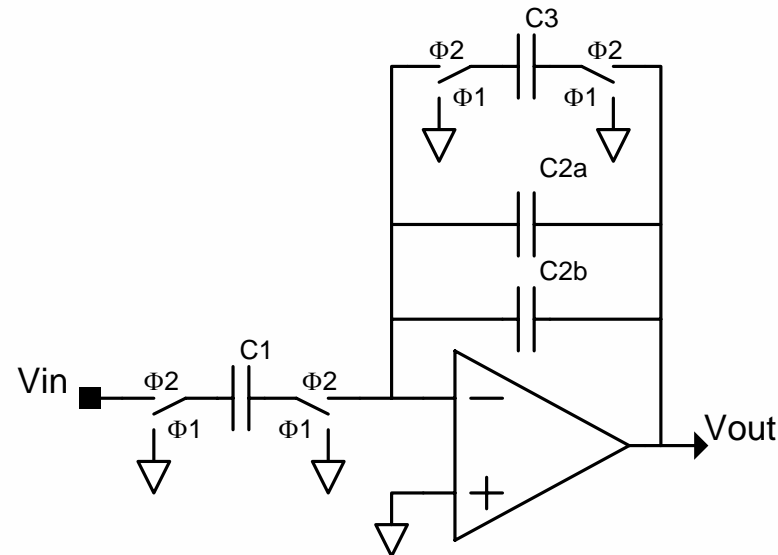

**Uses parallel combinations of available capacitors  
Many of Anadigm's CAM use this technique.**